ACADEMIC CENTRAL

PRACTICE EXAMINATION

NC(V) LEVEL 2

ELECTRONICS AND DIGITAL CONCEPTS FOR ROBOTICS

PAPER 2 · PRACTICE A · MARKING GUIDELINE

MARKS: 100

Marking guideline for the Academic Central NC(V) Level 2 Electronics and Digital Concepts for Robotics paper 2 · practice a.

Written by Academic Central for practice, following the NC(V) subject guidelines for NC(V) Level 2. It is not a Department of Higher Education and Training marking guideline.

How to mark: each ✓ is one mark. Give marks for the formula, the substitution and the answer with the correct unit. Use consistent accuracy. Accept other correct answers and neat, recognisable sketches.

SECTION A

QUESTION 1

1.1 D ✓
1.2 B ✓
1.3 C ✓
1.4 A ✓
1.5 B ✓
1.6 D ✓
1.7 A ✓
1.8 C ✓
1.9 C ✓
1.10 A ✓

(10 × 1) [10]

QUESTION 2

2.1 True ✓
2.2 False ✓
2.3 True ✓
2.4 False ✓
2.5 True ✓
2.6 True ✓
2.7 True ✓
2.8 False ✓
2.9 True ✓
2.10 False ✓

(10 × 1) [10]

QUESTION 3

3.1 J ✓
3.2 G ✓
3.3 D ✓
3.4 A ✓
3.5 C ✓
3.6 I ✓
3.7 E ✓

3.8 B ✓

3.9 F ✓

3.10 H ✓

(10 × 1) [10]


TOTAL SECTION A: [30]

SECTION B

QUESTION 4

4.1 (a) 2,2 kΩ ✓ (b) 45 mA ✓ (c) 3 300 000 Ω ✓ (d) 0,015 F ✓ (4)

4.2

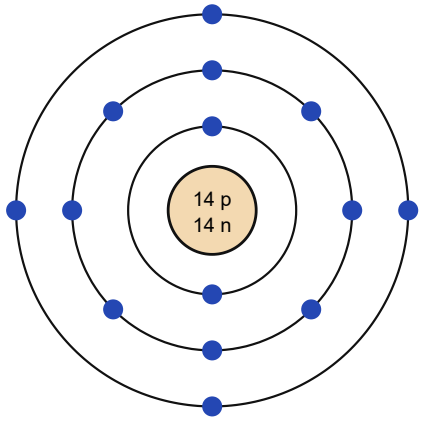

(Nucleus labelled (14 protons and 14 neutrons) 1; first shell 2 electrons 1; second shell 8 electrons 1; outer (valence) shell 4 electrons 1)

(4)

4.3 Copper has many free electrons that are loosely held and can move easily when a voltage is applied ✓✓; rubber has almost no free electrons – its electrons are tightly bound, so current cannot flow ✓✓. (4)

4.4 Any FOUR stages in order ✓✓✓✓: generation at the power station (about 22 kV); step-up transformer to very high voltage (e.g. 400 kV); transmission lines (national grid); substation steps the voltage down; distribution lines; pole / mini-substation transformer to 230 V; service connection and meter to the house (4)

[16]

QUESTION 5

5.1.1 $I = P \div V$ ✓ $= 40 \div 230 = 0{,}17\ A$ ✓ (2)

5.1.2 $R = V^2 \div P$ ✓ $= 230^2 \div 40 = 1\,322{,}5\ \Omega$ ✓ (or $V \div I$) (2)

5.1.3 $W = P \times t$ ✓ $= 40 \times 600\ s$ ✓ $= 24\,000\ J$ ✓ (3)

5.1.4 $E = 0{,}04\ kW \times 30\ h = 1{,}2\ kWh$ ✓✓; cost $= 1{,}2 \times R3{,}20 = R3{,}84$ ✓ (3)

5.2.1 $R_P = (12 \times 4) \div (12 + 4)$ ✓ $= 3\ \Omega$ ✓; $R_T = 6 + 3$ ✓ $= 9\ \Omega$ ✓ (4)

5.2.2 $I = V \div R \checkmark = 9 \div 9 = 1\ A \checkmark$ (2)

5.2.3 $V_P = I \times R_P \checkmark = 1 \times 3 = 3\ V \checkmark$ (2)

[18]


QUESTION 6

6.1 (a) yellow ✓, violet, brown, gold ✓ (b) red, red ✓, orange, silver ✓ (4)

6.2 (a) Series: $V = 6 \times 1{,}5 = 9\ V \checkmark$, $I = 0{,}5\ A \checkmark\checkmark$ (b) each group: $3 \times 1{,}5 = 4{,}5\ V$ ✓; two groups in parallel: $V = 4{,}5\ V$, $I = 2 \times 0{,}5 = 1\ A \checkmark\checkmark$ (6)

6.3 Pure silicon is doped (impurities added) ✓. N-type: a pentavalent impurity (5 valence electrons, e.g. phosphorus, arsenic) adds free electrons ✓✓. P-type: a trivalent impurity (3 valence electrons, e.g. boron, gallium) creates holes ✓ (4)

6.4

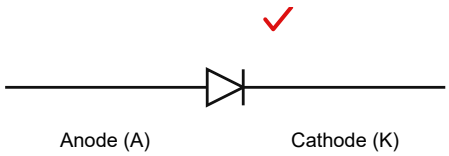


(Correct symbol with anode and cathode 1. Forward bias: anode more positive than cathode, the diode conducts (after about 0,7 V) 2. Reverse bias: cathode more positive, the diode blocks current 1)

(4)

[18]

QUESTION 7

7.1

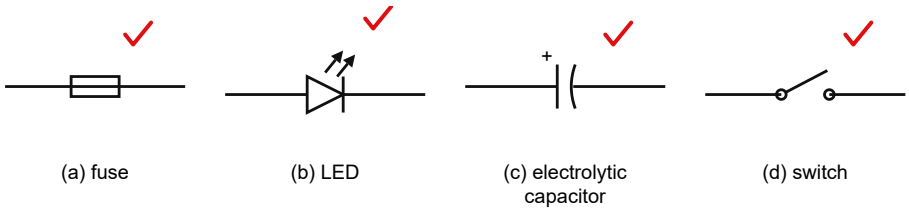

((a) fuse – rectangle with a line through it 1; (b) LED – diode symbol with two arrows pointing away 1; (c) electrolytic capacitor – one straight and one curved plate with + 1; (d) switch – a break in the line with a hinged contact 1)

(4)

7.2 Any SIX in order ✓✓✓✓✓✓: clean the board and component leads; insert the component through the holes; heat the copper strip and the lead together with a clean, tinned tip; feed solder onto the joint (not the iron) until it flows; remove the solder, then the iron; let the joint cool without moving it; trim the excess lead; inspect for a shiny cone-shaped joint and no bridges (6)

7.3 Any TWO ✓✓: keep the iron in its stand; work in a ventilated area (fumes); wear safety glasses; do not touch the tip; switch off and unplug after use; wash hands (lead solder) (2)

7.4 Read the colour code to find the nominal value and tolerance ✓; switch the multimeter to the correct resistance range ✓; make sure the resistor is not in a powered circuit / remove one leg ✓; measure without touching both leads with your fingers ✓; calculate the allowed range (e.g. 470 Ω ± 5% = 446,5 Ω to 493,5 Ω) ✓; the resistor is good if the reading is inside the range ✓ (6)

[18]

TOTAL SECTION B: [70]

TOTAL: 100

END OF MARKING GUIDELINE